 


SACRAMENTO STATE

Name: Karthik Shekarappa Email: karthikms@csus.edu Instructor: Dr. Behnam Arad

Course: EEE 273-Hierarchical Digital Design Methodology

Assignment Number: 3



```
module seq detect(input x,clk,rst, output reg Z);
reg[1:0] current_state, next_state;
parameter [1:0] \overline{IDLE} = 2'b00, s0 = 2'b01, s1 = 2'b10;
always@(posedge clk , negedge rst)
begin
      if(!rst)
                  current state <= IDLE;</pre>
      else
                  current state <= next state;</pre>
end
always@(*)
begin
next state = IDLE;
      case(current_state)
            IDLE:
                  begin
                        if(x)begin
                              next state = s0; Z = 1'b0;
                              end
                        else begin
                              next state = IDLE; Z = 1'b0;
                  end
            s0:
                  begin
                        if(!x)begin
                              next_state = s1; Z = 1'b0;
                              end
                        else begin
                              next state = s0; Z = 1'b0;
                              end
                  end
            s1:
                  begin
                        if(x) begin
                              next state = s0; Z = 1'b1;
                              end
                        else begin
                              next state = IDLE; Z = 1'b0;
                              end
                  end
            default: begin
                        next state = IDLE; Z = 1'b0;
                     end
      endcase
end
endmodule
```

```
`include "seqdetector.v";
module seqdetector fixture;
reg x,clk,rst;
reg [31:0]in;
wire Z;
integer i;
seq detect U1(.x(x), .Z(Z), .clk(clk), .rst(rst));
      monitor(stime, "X = %b, Z = %b, reset = %b\n", x, Z, rst);
initial
        $vcdpluson;
initial begin
in = 32'b101101010101010101010101010111011;
      for (i=0; i<32; i=i+1) begin
            @(posedge\ clk)\ x = in[i];end
end
initial
begin
        rst = 1'b1; x = 1'b1;
      #80 \text{ rst} = 1'b0;
      #70 \text{ rst} = 1'b1;
      #100 \text{ rst} = 1'b0;
end
initial
begin
       clk = 1'b1;
       forever #5 clk = ~clk;
end
initial
begin
       #800 $finish;
end
endmodule
```

Chronologic VCS simulator copyright 1991-2014 Contains Synopsys proprietary information. Compiler version I-2014.03-2; Runtime version I-2014.03-2; Feb 22 18:04 2019

VCD+ Writer I-2014.03-2 Copyright (c) 1991-2014 by Synopsys Inc.

$$0 X = 1 , Z = 0 , reset = 1$$

$$20 X = 0$$
 , $Z = 0$, reset = 1

30
$$X = 1$$
 , $Z = 1$, reset = 1

$$40 X = 1 , Z = 0 , reset = 1$$

$$60 X = 0$$
 , $Z = 0$, reset = 1

$$70 X = 1$$
 , $Z = 1$, reset = 1

$$80 X = 0$$
 , $Z = 0$, reset = 0

$$90 X = 1 , Z = 0 , reset = 0$$

$$100 X = 0$$
 , $Z = 0$, reset = 0

110
$$X = 1$$
 , $Z = 0$, reset = 0

120
$$X = 0$$
 , $Z = 0$, reset = 0

130
$$X = 1$$
 , $Z = 0$, reset = 0

$$140 X = 0$$
 , $Z = 0$, reset = 0

150
$$X = 0$$
 , $Z = 0$, reset = 1

160
$$X = 1$$
 , $Z = 0$, reset = 1

$$170 X = 0$$
 , $Z = 0$, reset = 1

180
$$X = 1$$
 , $Z = 1$, reset = 1

190
$$X = 0$$
 , $Z = 0$, reset = 1

$$200 X = 1$$
 , $Z = 1$, reset = 1

$$210 X = 0$$
 , $Z = 0$, reset = 1

$$220 X = 1 , Z = 1 , reset = 1$$

$$230 X = 0$$
 , $Z = 0$, reset = 1

$$240 X = 1$$
 , $Z = 1$, reset = 1

$$250 X = 0$$
 , $Z = 0$, reset = 0

$$260 X = 1 , Z = 0 , reset = 0$$

270 X = 0 , Z = 0 ,reset = 0 280 X = 1 , Z = 0 ,reset = 0 300 X = 0 , Z = 0 ,reset = 0

310 X = 1 , Z = 0 , reset = 0

\$finish called from file "seqdetector_fixture.v", line 32. \$finish at simulation time 800

VCS Simulation Report

Time: 800

CPU Time: 0.350 seconds; Data structure size: 0.0Mb

Fri Feb 22 18:04:09 2019